



Funded by
the European Union

Electric load

Alen Begović, full professor
Džemal Bijedić University of Mostar– Faculty of mechanical engineering

Electrical engineering 15.04.2025

"Funded by the European Union. Views and opinions expressed are however those of the author(s) only and do not necessarily reflect those of the European Union. Neither the European Union nor the granting authority can be."

**Partnership for Promotion and Popularization of Electrical Mobility through
Transformation and Modernization of WB HEIs Study Programs/PELMOB**

Call: ERASMUS-EDU-2022-CBHE-STRAND-2

Project Number: 101082860


Description and types

- An electrical load is an electrical component or portion of a circuit that consumes electric power, i.e. elements that take electrical energy from the source and convert it into another form of energy.
- We classify them into:
- resistive, they irreversibly and permanently convert electrical energy obtained from a source into thermal energy;
- capacitive, they convert electrical energy obtained from a source into electrostatic field energy;
- inductive, they convert electrical energy obtained from a source into electromagnetic field energy.

Direct current resistance


- Electrical loads behave differently in DC circuits, in terms of providing resistance to the current:
- a resistor behaves as a load that permanently and irreversibly converts the electrical energy of the source into heat; its resistance is finite;
- a capacitor behaves as an open circuit; its resistance is infinitely large;
- a coil behaves as a short circuit of the circuit; its resistance is zero.

Resistors connected in series

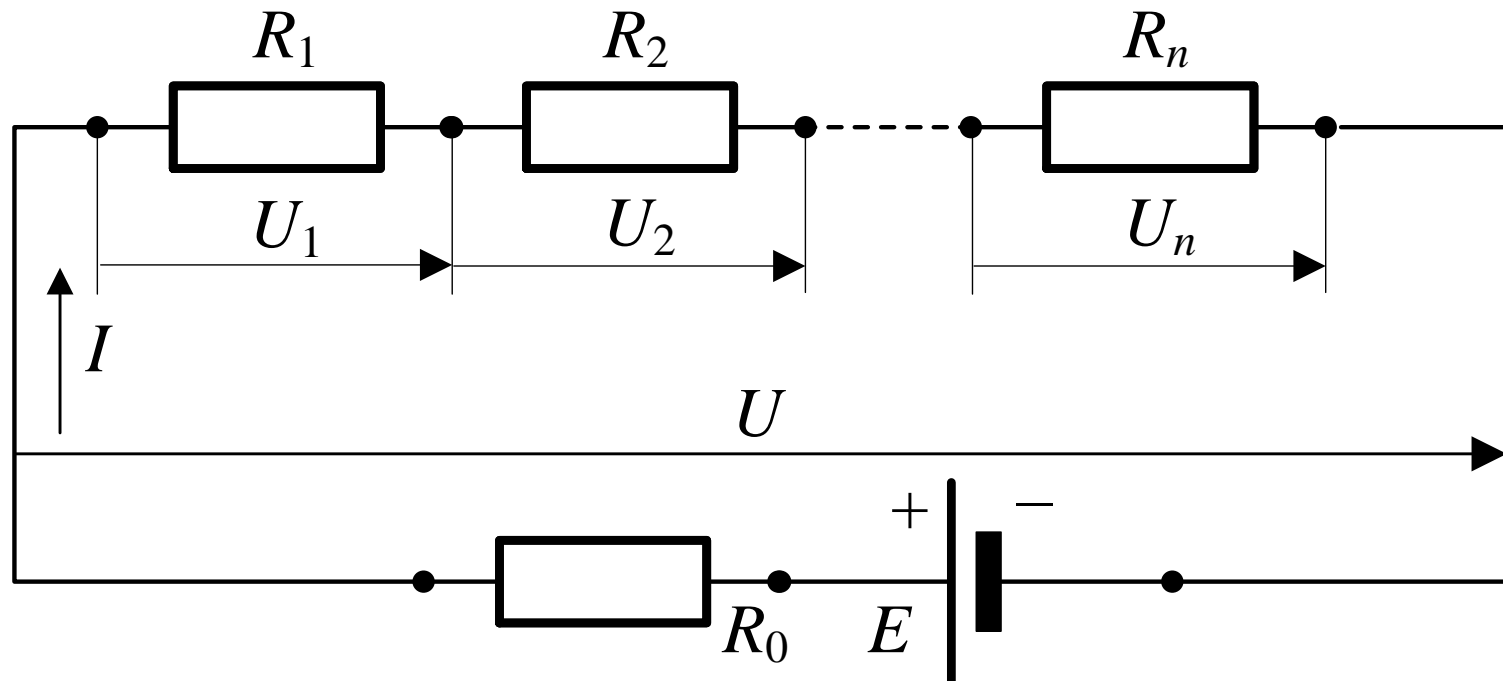



$$R_{\text{ek}} = \sum_{k=1}^n R_k = R_1 + R_2 + \dots + R_n$$

Resistors connected in parallel

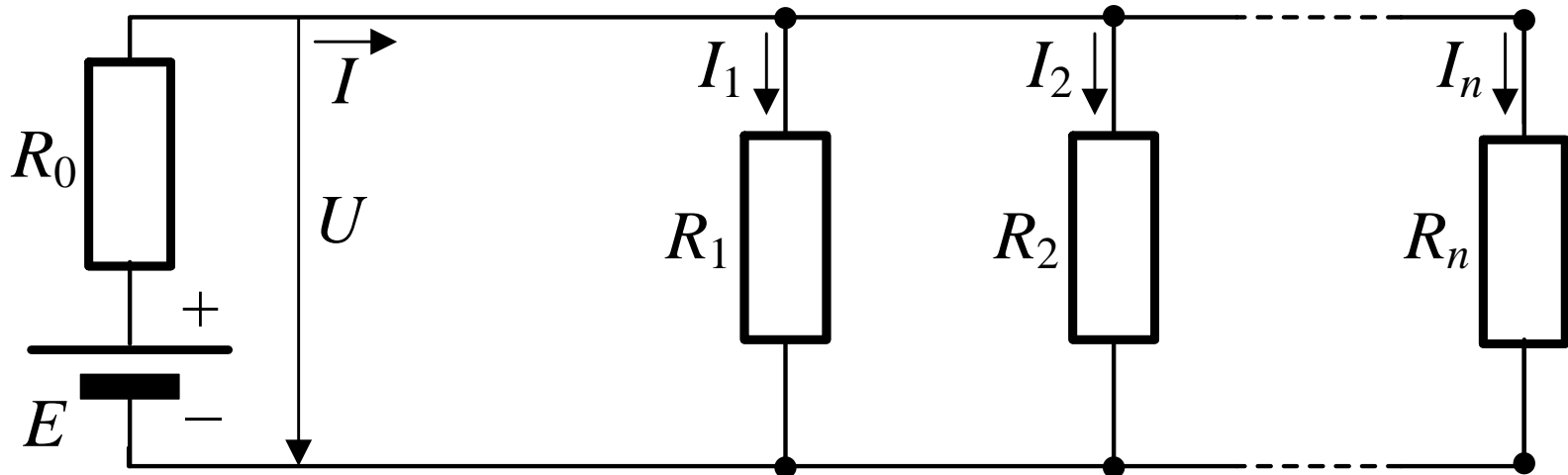

$$\frac{1}{R_{ek}} = \sum_{k=1}^n \frac{1}{R_k} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$

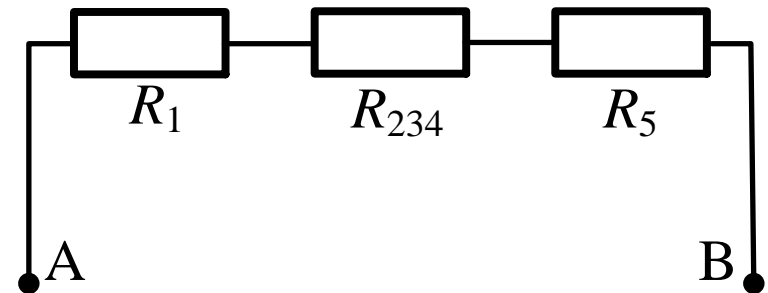
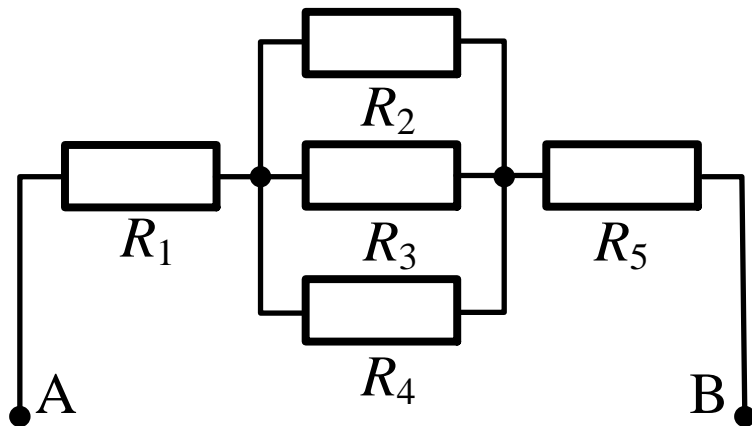
Resistors connected arbitrarily – example 1



$$\frac{1}{R_{234}} = \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}$$

$$R_{AB} = R_1 + R_{234} + R_5$$

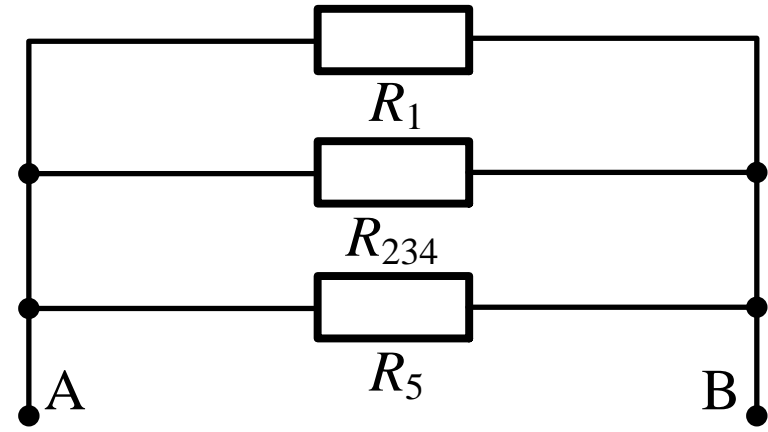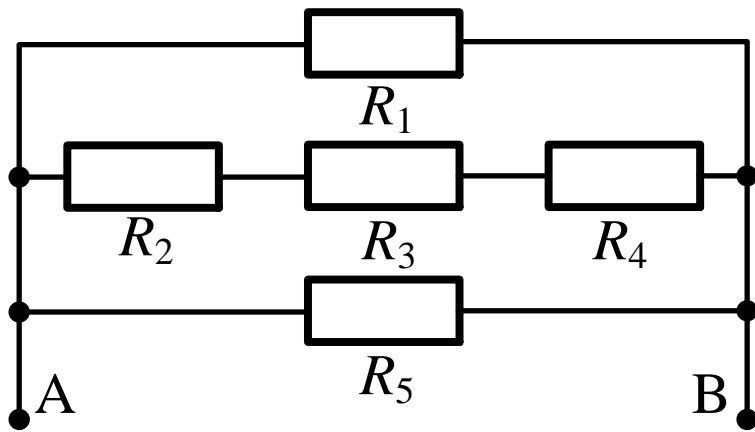
Resistors connected arbitrarily – example 2




$$R_{234} = R_2 + R_3 + R_4$$

$$\frac{1}{R_{AB}} = \frac{1}{R_1} + \frac{1}{R_{234}} + \frac{1}{R_5}$$

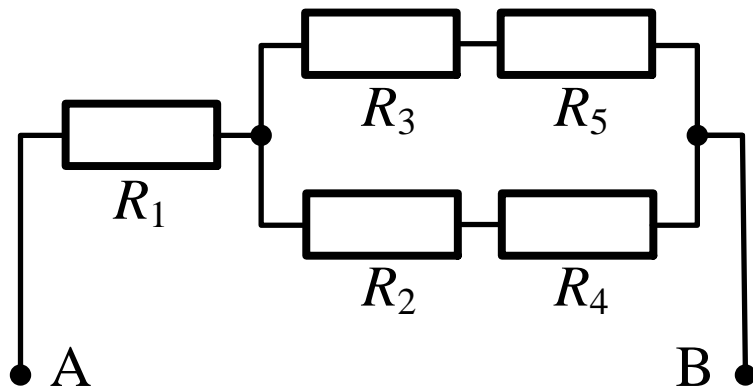
Resistors connected arbitrarily – example 3


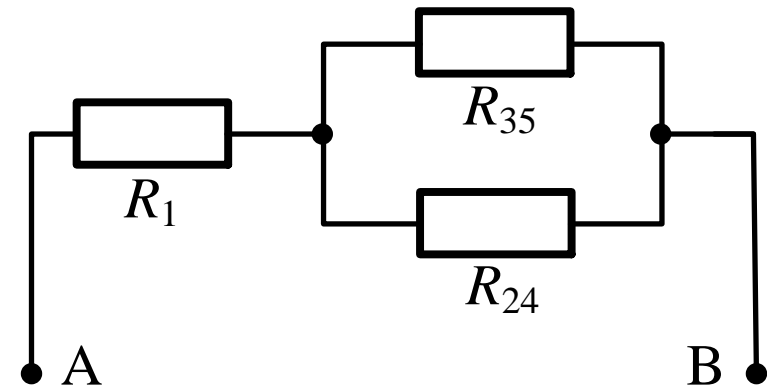
$$R_{24} = R_2 + R_4 \quad R_{35} = R_3 + R_5$$



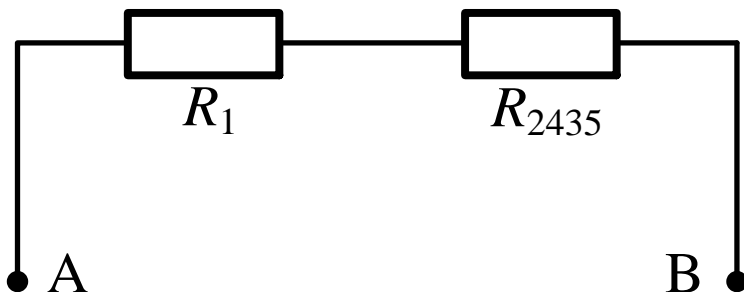
$$\frac{1}{R_{2435}} = \frac{1}{R_{24}} + \frac{1}{R_{35}}$$



$$R_{AB} = R_1 + R_{2435}$$

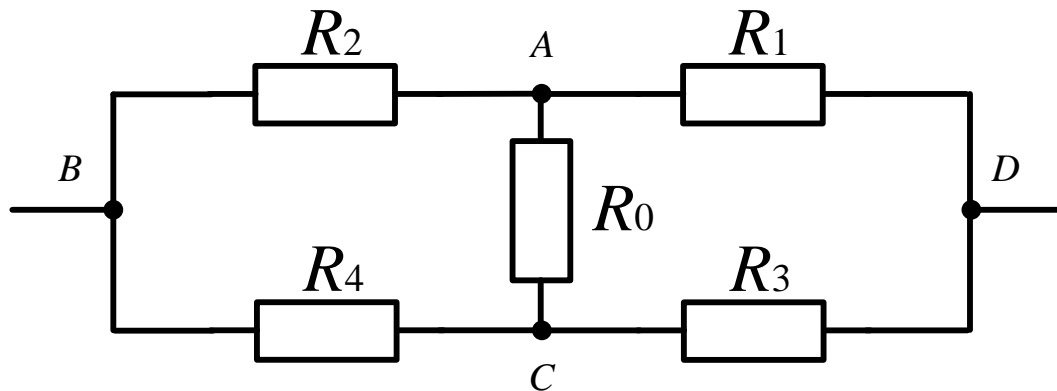Resistors connected arbitrarily – example 4




$$R_{24} = R_2 + R_4 \quad R_{13} = R_1 + R_3$$

$$\frac{1}{R_{AC}} = \frac{1}{R_0} + \frac{1}{R_{13}} + \frac{1}{R_{24}} = \frac{1}{R_0} + \frac{1}{R_1 + R_3} + \frac{1}{R_2 + R_4}$$

- Izračun otpornosti R_{BD} nije tako jednostavan.

Transform delta-star

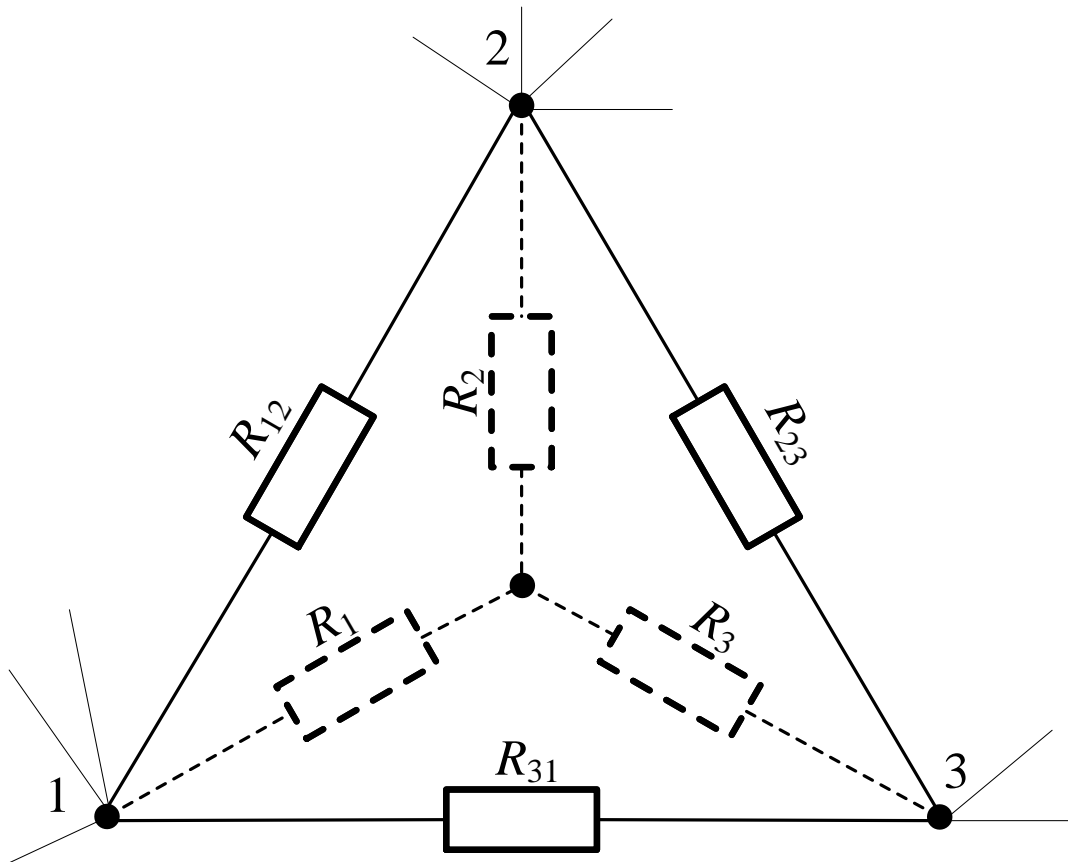


$$R_1 = \frac{R_{31} R_{12}}{R_{12} + R_{23} + R_{31}}$$

$$R_2 = \frac{R_{12} R_{23}}{R_{12} + R_{23} + R_{31}}$$

$$R_3 = \frac{R_{23} R_{31}}{R_{12} + R_{23} + R_{31}}$$

Transform star-delta

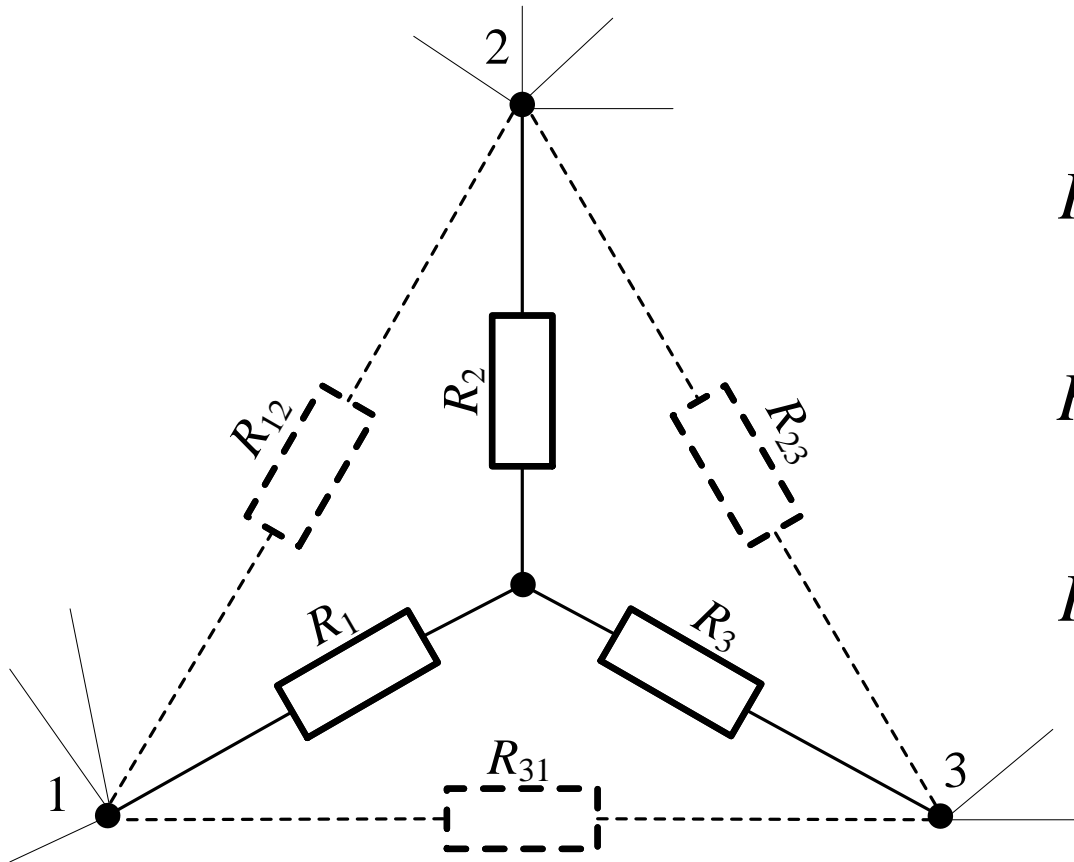


$$R_{12} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$R_{23} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_{31} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

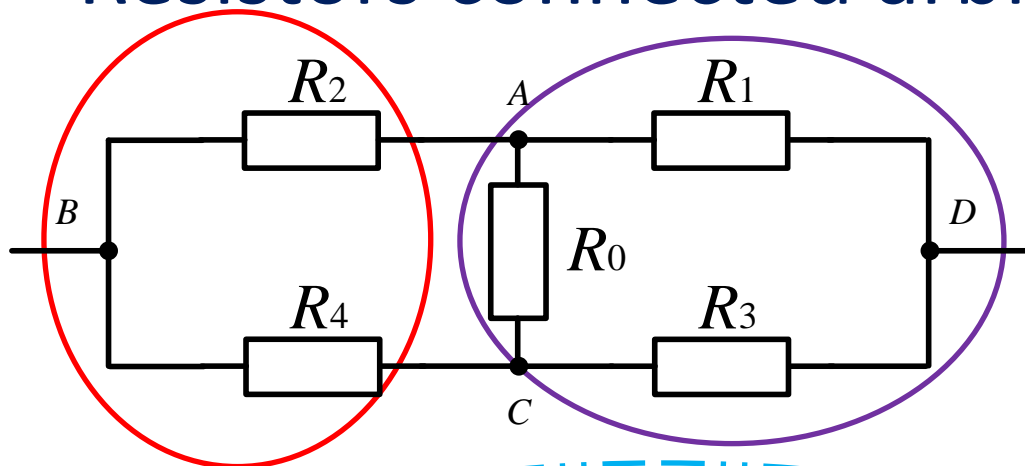
Resistors connected arbitrarily – example 5




$$R_{01} = \frac{R_0 R_1}{R_0 + R_1 + R_3}$$

$$R_{03} = \frac{R_0 R_3}{R_0 + R_1 + R_3}$$
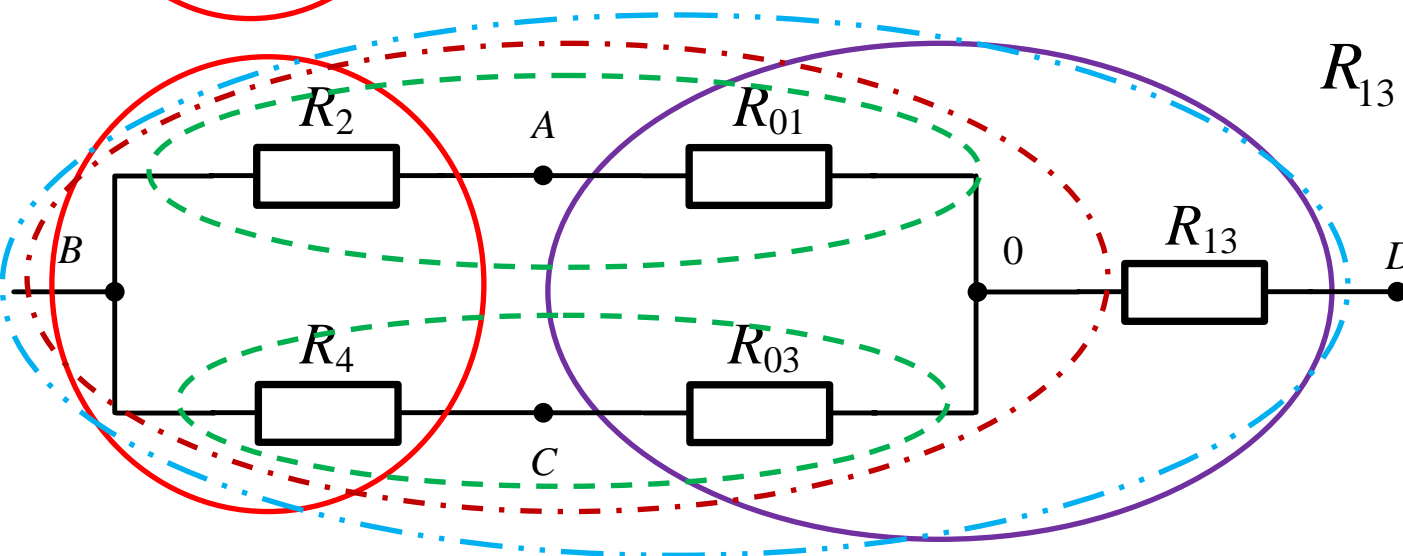
$$R_{13} = \frac{R_1 R_3}{R_0 + R_1 + R_3}$$



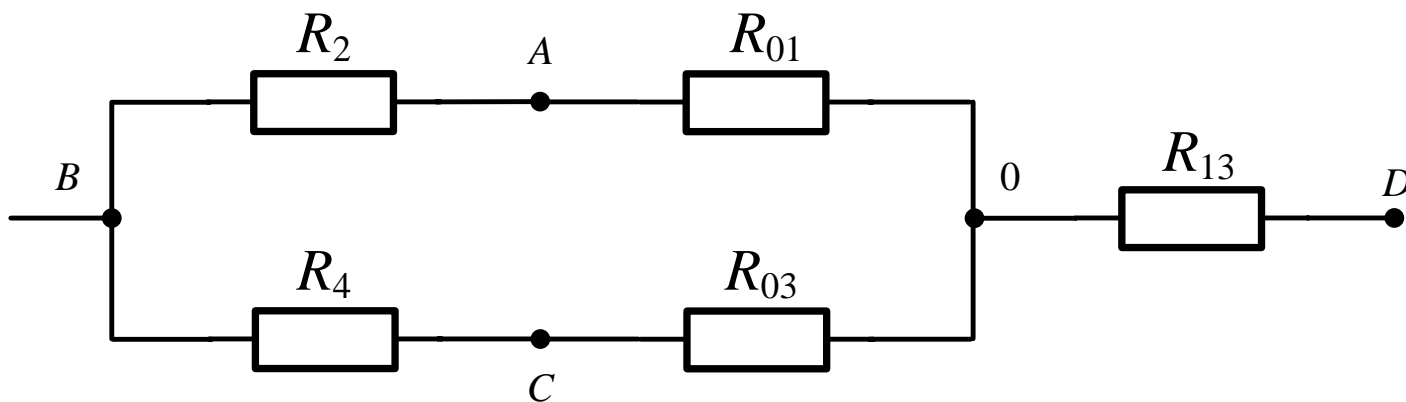Resistors connected arbitrarily – example 5



$$R_{201} = R_2 + R_{01}$$

$$R_{403} = R_4 + R_{03}$$

$$\frac{1}{R_{B0}} = \frac{1}{R_{201}} + \frac{1}{R_{403}}$$

$$R_{BD} = R_{B0} + R_{13} = \frac{(R_2 + R_{01})(R_4 + R_{03})}{R_2 + R_{01} + R_4 + R_{03}} + R_{13}$$